 


VE370_Lab4

Group 2: Huang Han, Ye Zixin, Yuan Haotong

Modeling and Implementation

Based on the pipeline done in Lab 3, we have added hazard detection mechanisms for data hazards and control hazards. The overall circuit is shown below:



1. Data Hazard Detection and Resolution

1.1 Data Forwarding Unit (Forwarding_unit.v)

Resolves RAW dependencies through forwarding:

- **EX-EX Forwarding:** Forwards EX/MEM results to EX stage inputs
- **MEM-EX Forwarding:** Forwards MEM/WB results to EX stage inputs
- Control signals: `data_hazard_A/B` (2'b00=no forwarding, 2'b01=MEM forwarding, 2'b10=EX forwarding)

1.2 JALR Forwarding Logic

Handles JALR instructions depending on JAL results:

- Detects if JALR's rs1 register matches JAL's destination register

- Provides JAL's PC+4 value directly as JALR base address

1.3 Load-Use Hazard Detection (Data_Hazard_Control)

Detects load-use hazards and inserts pipeline stalls:

- Checks register dependencies between load instructions in ID/EX stage and current instruction
- When hazard detected: sets `PCWRITE=0` and `load_IF_ID_Write=0` to stall pipeline

2. Control Hazard Detection and Resolution

2.1 Control Hazard Detection (Control_Hazard)

Uses predict-not-taken strategy for branches and jumps:

- Tracks branch state with `branch_taken_prev` register to avoid duplicate flushes
- When branch taken or jump instruction encountered:
 - `IF_Flush = 1`: Flush IF/ID register
 - `PCSrc = 1`: Select jump target address
 - `ctrl_IF_ID_Write = 0`: Insert pipeline bubble

3. Memory Address Hazard Detection

3.1 Memory Address Hazard (Memory_Address_Hazard.v)

Handles hazards between consecutive memory operations:

- **Store-Load Forwarding**: Forwards store data when consecutive store/load access same address
- **Load-Store Forwarding**: Forwards load result when used immediately as store data

4. Integrated Hazard Control

4.1 Priority and Interaction

1. **Control hazards**: Highest priority (branches/jumps)
2. **Load-use hazards**: Cause pipeline stalls
3. **Data forwarding**: Resolves most RAW hazards without stalling

4.2 Combined Control Signals

- `final_IF_ID_Write = ctrl_IF_ID_Write & load_IF_ID_Write`: Combines control and load hazard signals
- Early branch resolution in ID stage reduces control hazard penalty to 1 cycle

5. Key Monitoring Signals

Data Hazard Signals:

- `data_hazard_A/B[1:0]`: Forward control (2'b00=none, 2'b01=MEM, 2'b10=EX)
- `Hazard`: Load-use hazard detected
- `PCWRITE/load_IF_ID_Write`: Pipeline stall controls

Control Hazard Signals:

- **branch_taken**: Branch condition result
- **IF_Flush**: Flush IF/ID register
- **PCSrc**: PC source selection (0=PC+4, 1=target)

Pipeline State:

- **PC_cs[31:0]**: Current PC value
- **IDEX_rs1/rs2_addr_out[4:0]**: Source registers
- **EXMEM/MEMWB_rd_addr_out[4:0]**: Destination registers

Simulation Result

Hazard Detection Test Cases

Following the instruction sequence in **Lab4_testcase.s**, we analyze hazards in execution order:

Hazard 1: Store Data Forwarding


```
addi t1, x0, 0x399      # PC=0x00: t1 = 0x399
sw t1, 4(x0)            # PC=0x04: uses t1 as store data (EX-EX forwarding)
```

Hazard Type: RAW data hazard (store data forwarding)

Resolution: EX-EX forwarding via Forwarding_unit

Wire Signal Values:

- **data_hazard_B** = 2'b10 (EX forwarding for store data)
- **EXMEM_RegWrite_out** = 1 (EX/MEM stage writing t1)
- **EXMEM_rd_addr_out** = 5'b00110 (t1 = x6)
- **IDEX_rs2_addr_out** = 5'b00110 (sw reads t1)
- **ALU_input2_forwarded** uses forwarded data from EX/MEM stage

 

Hazard 2: Load-Use Data Hazard


```
lb t0, 4(x0)            # PC=0x08: t0 = 0xffff_ff99 (load instruction)
sw t0, 0(x0)            # PC=0x0C: uses t0 immediately (stall required)
```

Hazard Type: Load-use data hazard

Resolution: Pipeline stall inserted by Data_Hazard_Control module

Wire Signal Values:

- **Hazard = 1** (hazard detected)
- **PCWRITE = 0** (stall PC)
- **load_IF_ID_Write = 0** (stall IF/ID register from Data_Hazard_Control module)
- **IDEX_MemRead_out = 1** (load in EX stage)
- **IDEX_rd_addr_out = 5'b00101** (t0 = x5)
- **IFID_Inst_out[24:20] = 5'b00101** (sw uses t0 as rs2)
- **final_IF_ID_Write = 0** (combined stall signal)

 

Hazard 3: Control Hazard - Branch Not Taken


```
beq t1, x0, wrong_branch # PC=0x10: should not branch (t1 = 0x399 ≠ 0)
lw t3, 0(x0)             # PC=0x14: next instruction executed normally
```

Hazard Type: Control hazard (branch not taken)

Resolution: Predict-not-taken strategy works correctly

Wire Signal Values:

- **branch_taken = 0** (branch condition false)
- **Branch = 1** (branch instruction detected)
- **IF_Flush = 0** (no flush needed)
- **PCSrc = 0** (continue with PC+4)
- **PC_cs = 0x14** (continues to next instruction)

 

Hazard 4: Load-Use with Branch Operand

```
lw t3, 0(x0)             # PC=0x14: t3 = 0xffff_ff99 (load instruction)
bne t0, t3, wrong_branch # PC=0x18: uses t3 immediately (stall + forwarding)
```


Hazard Type: Load-use hazard + Control hazard

Resolution: Pipeline stall + Branch evaluation with forwarded data

Wire Signal Values:

- **Hazard = 1** (load-use hazard for t3)
- **PCWRITE = 0, load_IF_ID_Write = 0** (stall pipeline)
- **IDEX_MemRead_out = 1** (load in EX stage)

- `IDEX_rd_addr_out` = 5'b11100 (t3 = x28)
- `IFID_Inst_out[24:20]` = 5'b11100 (bne uses t3 as rs2)
- After stall: `data_hazard_B` = 2'b01 (MEM forwarding for t3)
- `branch_taken` = 0 (branch condition false: t0 == t3)
- `IF_Flush` = 0 (no flush needed)

 

Hazard 5: EX-EX Data Forwarding


```
add t2, t0, t3      # PC=0x1C: t2 = 0xffff_ff32
and t1, t2, t3      # PC=0x20: uses t2 immediately (EX-EX forwarding)
```

Hazard Type: RAW data hazard

Resolution: EX-EX forwarding via Forwarding_unit

Wire Signal Values:

- `data_hazard_A` = 2'b10 (EX forwarding for t2)
- `EXMEM_RegWrite_out` = 1 (EX/MEM stage writing t2)
- `EXMEM_rd_addr_out` = 5'b00111 (t2 = x7)
- `IDEX_rs1_addr_out` = 5'b00111 (and reads t2)
- `data_hazard_B` = 2'b00 (MEM forwarding for t3)

 

Hazard 6: MEM-EX Data Forwarding


```
andi t1, t2, 0      # PC=0x24: t1 = 0x0
sub t0, t1, x0       # PC=0x28: uses t1 immediately (MEM-EX forwarding)
```

Hazard Type: RAW data hazard

Resolution: MEM-EX forwarding via Forwarding_unit

Wire Signal Values:

- `data_hazard_A = 2'b01` (MEM forwarding for t1)
- `MEMWB_RegWrite_out = 1` (MEM/WB stage writing t1)
- `MEMWB_rd_addr_out = 5'b00110` (t1 = x6)
- `IDEX_rs1_addr_out = 5'b00110` (sub reads t1)
- `data_hazard_B = 2'b00` (no forwarding for x0)
- `ALU_input1` uses forwarded data from MEM/WB stage in the last cycle.
- `ALU_input2 = 0` (x0 register value)

 

Hazard 7: Control Hazard - Branch Taken


```
bge t0, t1, right_branch # PC=0x2C: should branch (t0=0 ≥ t1=0)
add t2, x0, x0           # PC=0x30: wrong_branch (skipped due to branch)
```

Hazard Type: Control hazard (branch taken)

Resolution: Pipeline flush by Control_Hazard module

Wire Signal Values:

- `branch_taken = 1` (branch condition true: $0 \geq 0$)
- `if_Jump = 1` (whether it's the instruction of jal or jalr)
- `IF_Flush = 1` (flush IF/ID register)
- `PCSrc = 1` (select branch target)
- `PC_cs = 0x48` (current PC value)
- `PC_branch_target = 0x38` (calculated target address)

 

Hazard 8: JAL Instruction - Control and Data Hazard

```
jal x1, jump_test      # PC=0x38: right_branch, x1 = PC + 4 = 0x3C
or t3 t3 t2
jalr x0, x1, 0
jal x1, Exit           # PC=0x3C: next instruction (not executed)
```


Hazard Type: Control hazard (unconditional jump) + Data hazard (writes x1)

Resolution: Pipeline flush + Register write

Wire Signal Values:

- `if_Jump = 1` (jump instruction detected in the previous cycle)

- `IF_Flush = 1` (flush IF/ID register in the previous cycle)
- `PCSrc = 1` (select jump target in the previous cycle)
- `PC_cs = 0x48` (assume the branch not taken, current PC value, will be changed to 0x38 in the next cycle)
- `RegWrite = 1` (write PC+4 to x1)
- `IDEX_rd_addr_out = 5'b00001` (x1 register)
- `IDEX_if_Jump_out = 1` (jump signal in EX stage)
- `EX_result_mux_out = 0x3C` (PC + 4 value for writeback)

 

RTL schematic

here is the screenshor of the schematic, and the file can be found in [./schematic.pdf](#).

